

Lab4-Bonus (Timer)

***Lab 4: Timer, Hardware-based True
Random Number Generator, ROM-
based Game Access Control on FPGA***

Sohail Shareef Mohammed


ECE6370

1. How it Works?

“Lab 4 Bonus” project introduces many changes to the previous Lab 4 project. Here we have implemented reconfigurable timer to the game using two 7-segment display devices, where each digit is updated with 4 toggle switches. The timer can be set after the board is authenticated and that is triggered to reload by using the password entering button. The timer is a BCD timer and any value over 9 will be loaded to the timer as 9. The maximum value of the timer is 99 seconds. The timer starts to count down after the random number generator button is pushed. When the timer value reaches 0, the inputs from Player 2 are no longer taken. To play the next round, the timer reload button should be pushed before the random number generator button is pushed.

2. Block Diagram

Overall Architecture of the Game :

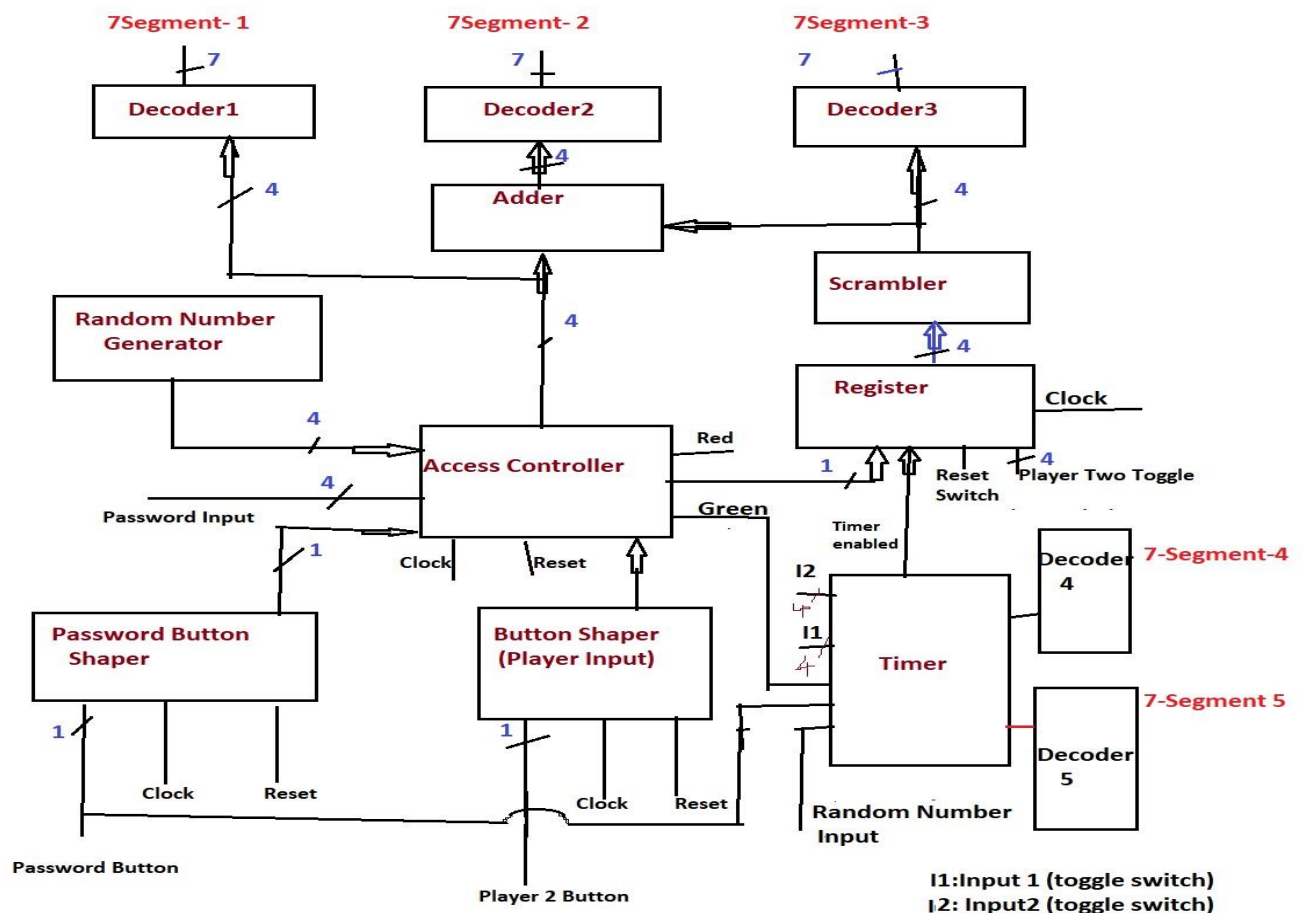


Timer, Hardware-based True Random Number Generator, ROM-based Game Access Control on FPGA

From the above Diagram it clearly Shows the flow and design of the architecture.


3. Verilog Modules (ModelSim)

3.0 Timer Module

 

This module count the number which user set till 0 .In this module first it check if pasw. is a authenticated and then on pressing the password authenticating button it will reload the toggle switch value on to counter. Once random number is pressed then it automatically will start to count. This can be reflected on two 7 segment display through decoders.

3.1 Scrambler Module

 


In this module we map every number between 0 and 15 to different number from 0-15 such that no two number has same number mapped. This module record all the mapping and it provide corresponding scrambled number of the requested number.

Mapping Index card for this particular example is as follows:


Unscrambled		Scrambled
0	→	D
1	→	7
2	→	4
3	→	0
4	→	F
5	→	8
6	→	1
7	→	C
8	→	6
9	→	E
A	→	3
B	→	A
C	→	5
D	→	2
E	→	9
F	→	B

3.2 ADDER

 


This module is used to find the sum of two 4 digit input signal. Here we are ignoring the carry bit. Output of the signal is 4 digit .One of the input signal is the output of scramble and other input is 1st Toggle switch.

3.3 DECODER 4x7

 

This module convert the 4 digit signal into 7 bit signal that support 7 Segment display. This signal is very important to understand te nature and make the city green.

3.5 Scramble

 

This module implements adder, scramble and decoder modules. In this module it accepts 2 input signal and output signal are 3. This module is top module it implement the main game logic. where one user has to guess the scrambled number.


3.5 Button Inversion:

This helps in generating a low pulse whenever the push button is pressed and the reset is set. If it is pressed $Pb_in_s = 0$ and if $Pb_in_s = 0$ then $Inv_sg_s = 1$ for one cycle called the single cycle pulse otherwise $Inv_sg_s = 0$ and that means that button has not been pushed. Basically converts a low pulse to a high pulse.



This shows all possible input and output of Button Inversion Test bench used .


3.6 Counter:

 

This Module will start counting when active-low reset is de-asserted and rolls over to 0 when it reaches its maximum value of 4'hF. It will keep counting as long as it is provided with a running clock and reset is held high.

 
3.7 ROM Module:

This module will save the values at different addresses. We can access the values by giving the address as input




If we give the address value at the input we get the value saved at that address as the output. Here in the diagram shows the address values.

3.8 Access Module:

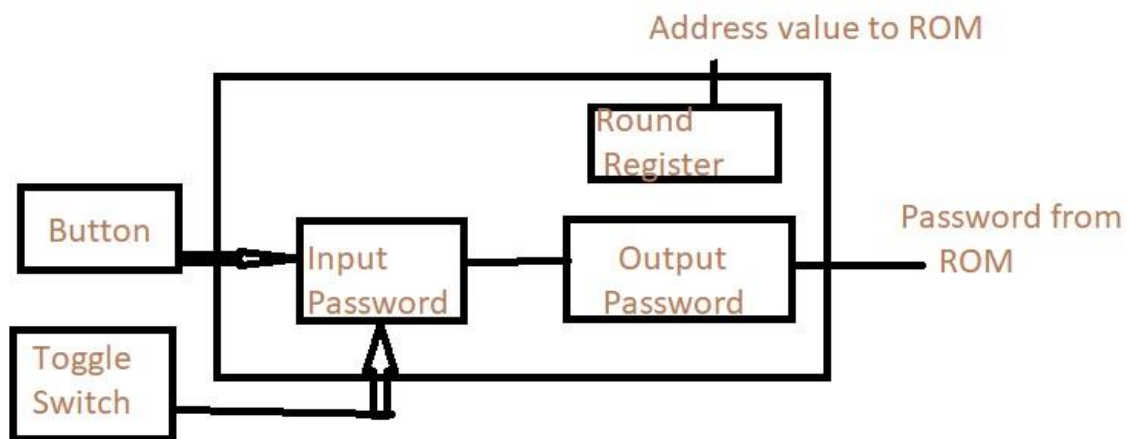

In this module when user press the button after resetting and setting the 4 bit password at each time ,the input password is compared with the password we got from the output password from ROM module. Thus we compare the input password with the password from ROM module here.

3.9 Random Number Generator

 

This module is combination of the button Inversion and Counter . Output of this module is the 4 bit Count value whereas the input is the signal.

Depending how long user press the button the module decides the counter values.

4. Waveforms

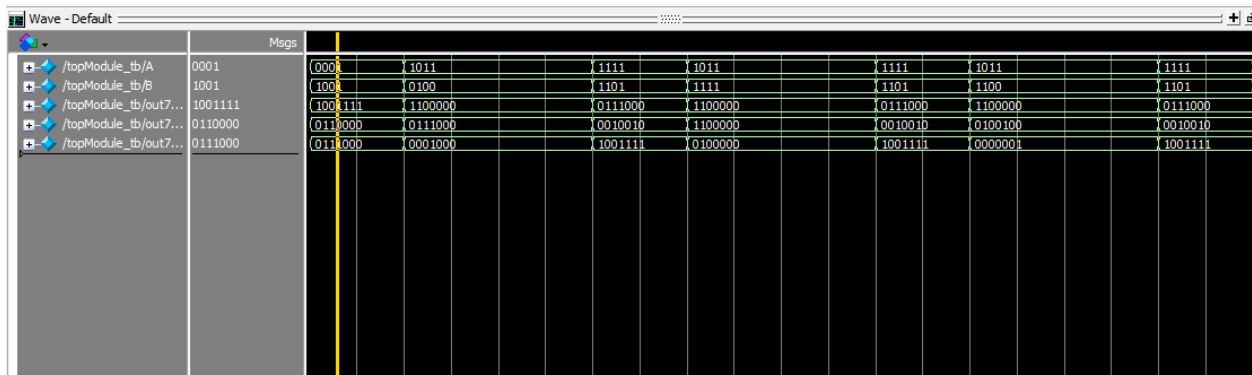


Figure 0: Adder module

As seen from waveform (Figure 1). In this graph the top module function applies all” scrambler top module” logics. From graph, for some of the examples we can see the output is F. this happen when we get sum 15 after addition of two signals. Getting “F” or 15 is the winning condition of this game.

Readings: $1001 + 0001$ (Scrambled) $\Rightarrow 1001 + 0110$ (Unscrambled) $= 1111$

 


Figure 1: Decoder -Output Waveform

From above Waveform, we can see that 4-bit numbers are being decoded to 7-bit numbers. This 7-bit numbers are helpful to send to 7 segment displays .

 


Figure 2: Scrambler -Output Waveform

From above waveform, we can see that every input of scrambler is mapped to unique new value in the output such that output range is in between 0 to 15.

 


Figure 3: Adder -Output Waveform

From Above waveform, different sum result of the different 4 digit number can be observed .

 


Figure 4: Button Inversion Waveform

From Above waveform, It can be seen generating a low pulse whenever the push button is pressed and the reset is set.

 


Figure 5: Counter Waveform

From Above waveform, Counter starts incrementing when pulse =1 and reset=1. It will reset when reset is zero or incase when pulse is 0.

 


Figure 6: Random Number Generator

This module shows that on low input pulse the input start incrementing once user release the button it stop counting and it will show the output as the counter number.

 


Figure 7: Access Control Waveform and ROM Password Module

This module will compare the password inserted by user and the password saved in the ROM module. Once the password is verified the Green Led will be ON and when password is not verified the red led is OFF.



Figure 1: ROM Module

This module will verify the address and saved values .

5 And Now its Game Time

I asked my roommates to play this game. Tabish Kamran and Zishan Amlani played this game. They are master's student in the field of Mechanical Engineering at UH. The Game rule remains the same and I

have set 5 matches and whoever wins most number of Games wins the Games. The secret mapping indexes card is showed to them for very short time to go through it .

Unscrambled		Scrambled
0	→	D
1	→	7
2	→	4
3	→	0
4	→	F
5	→	8
6	→	1
7	→	C
8	→	6
9	→	E
A	→	3
B	→	A
C	→	5
D	→	2
E	→	9
F	→	B

The Game Rule remain same , first player will verify his 16 bit password on the board and once he verify the password the Green LED will light up and incase of not verified the red LED will be ON. Once password is verified the player 1 will press the button, depend on how long he press button It will show the random number using the button and then player2 test will be to remember the scrambled number correspond to this number and set other number such that sum of 1st random number and 2nd person unscrambled number will be displayed in 3rd 7 segment display. If the result is 15 second player wins the game.This game will continue until it comes to common understanding

6 FPGA Screen Shot

Password Verification:

First user has to verify 16 bit password by entering 4 bit each time using toggle switch. and once password is verified he must make sure Green LED is ON (Green LED represent the password is verified and RED led represent that password is incorrect)

 


Figure 2: Green LED is ON (Password is verified).

Password not verified Incident:

 


Figure 3: RED LED is ON (password is not verified)

Random Number Generation:

Once password is verified he must again press password verification button to reload the input on to timer and after that user can long press the random number generator button. Depending on how long he presses a random number will be generated and displayed on the 7 segments and also the timer will start to count.


 


Figure 4: Random Number generation after long pressing button and timer initiation

Then player must now calculate how much number he must add to get sum of 15. But twist in the game is that user must give scrambled input of that number as input to the system. He has then to press the load button so that number get loaded on to the system.

Example 1:


If we assume player one has pressed the random number button and that is displayed on 7 segments as 9 and now player user calculate that he need to add 5 more to get the result but he can't give 6 directly rather he has to give scrambled input of 5. If we assume he remember correct mapping number of 6 which was for example was 8 then upon selecting the scrambled number using toggle switches we get the sum of the result on the 7segment.

 

Example 2:

If we assume that 1st person was unsuccessful to assume the right scrambled number which can also be seen in the 7Segment as the sum value on the 7Segment won't reflect the "F" value In such cases 1st person will loose points as he loss the game and meanwhile 2nd person gets extra points as he won the game again.

This can also be shown in below picture

 

7 Appendix

Module Design:

Timer Module

```
module t_timer(led,button_pulse,pulse,clk,rst,input1,input2,timerOutt1,timerOutt2,splayer);

    input clk,rst,pulse,led,button_pulse;
    input [3:0]input1,input2;
    //output reg [6:0] outSignal1,outSignal;
    output reg [3:0] timerOutt1,timerOutt2;
    output reg splayer;
    // reg [25:0] swire;
    reg [25:0] slow_clk;
    reg [3:0]timer1,timer2;
    reg flag=0;
```



```

reg flag1=0;
always @(posedge clk)
    begin
        if(rst == 0)
            begin
                timer1<=0;
                timer2<=0;
                slow_clk <= 0;
                flag=0;
                flag1=0;
                splayer=0;
            end
        else
            begin
                if(timer1 == 4'b0000 && timer2 == 4'b0000) begin
                    flag=0;
                    flag1=0;
                    splayer=0;
                end
                if(button_pulse==1 && led ==1) begin
                    timer1<=input2;
                    timer2<=input1;
                    flag=1;
                end
                if(pulse==1 && flag==1) begin
                    flag1=1;
                    splayer=1;
                end
                if(flag1==1) begin

```

```

if(timer1 > 4'b1001) begin
    timer1<= 4'b1001;
end

if(timer2 > 4'b1001) begin
    timer2<= 4'b1001;
end

if (slow_clk == 26'd50000000) begin
    if(timer1==4'b0000) begin
        timer2 <= timer2 - 1'b1;
    end

    timer1 <= timer1 - 1'b1;

    slow_clk<= 0;
end

else begin
    slow_clk <= slow_clk + 1'b1;
end

if(timer1 > 4'b1001) begin
    timer1<= 4'b1001;
end

if(timer2 > 4'b1001) begin
    timer2<= 4'b1001;
end

end

timerOutt1=timer2;
timerOutt2=timer1;
//assign swire=slow_clk;

```

```
                end
            end
        end
    end
endmodule
```

Adder Module

```
// ECE6370
// Author: Sohail Shareef Mohammed - 5985
// Application : Adder Function calculate the sum of the two 4-bit numbers.
module full_add( a ,b ,sum );
    output [4:0]sum ;
    input [3:0]a ;
    input [3:0]b ;
    assign sum = a + b;
endmodule
```

Scramble Module

```
/ ECE6370
// Author: Sohail Shareef Mohammed - 5985
// Application : This will map every number between 0 to 15 to someother unique number between 0 to 15. This mapping will be done in accordance to index card.
module scrambler(unScrambled,scrambled);

    input [3:0]scrambled;
    output [3:0]unScrambled;
    reg [3:0]unScrambled;

    always @(scrambled)
        begin
```

```

        case(scrambled)
            4'b0000: begin unScrambled =4'b1101;end
            4'b0001: begin unScrambled =4'b0111;end
            4'b0010: begin unScrambled =4'b0100;end
            4'b0011: begin unScrambled =4'b0000;end
            4'b0100: begin unScrambled =4'b1111;end
            4'b0101: begin unScrambled =4'b1000;end
            4'b0110: begin unScrambled =4'b0001;end
            4'b0111: begin unScrambled =4'b1100;end
            4'b1000: begin unScrambled =4'b0110;end
            4'b1001: begin unScrambled =4'b1110;end
            4'b1010: begin unScrambled =4'b0011;end
            4'b1011: begin unScrambled =4'b1010;end
            4'b1100: begin unScrambled =4'b0101;end
            4'b1101: begin unScrambled =4'b0010;end
            4'b1110: begin unScrambled =4'b1001;end
            4'b1111: begin unScrambled =4'b1011;end
            default: begin unScrambled =4'b0000;end
        endcase
    end
endmodule

```

Decoder Module

// ECE6370

// Author: Sohail Shareef Mohammed - 5985

// Application : This will convert 4-bit BCD to 7 bit binary number such that it is compatible to 7 segment display

```
module decoder4to7(inpSignal,outSignal);
```

```

input [3:0]inpSignal;
output [6:0]outSignal;
reg [6:0]outSignal;

always @(inpSignal)
    begin
        case(inpSignal)
            4'b0000: begin outSignal =7'b0000001;end
            4'b0001: begin outSignal =7'b1001111;end
            4'b0010: begin outSignal =7'b0010010;end
            4'b0011: begin outSignal =7'b0000110;end
            4'b0100: begin outSignal =7'b1001100;end
            4'b0101: begin outSignal =7'b0100100;end
            4'b0110: begin outSignal =7'b0100000;end
            4'b0111: begin outSignal =7'b0001111;end
            4'b1000: begin outSignal =7'b0000000;end
            4'b1001: begin outSignal =7'b0000100;end
            4'b1010: begin outSignal =7'b0001000;end
            4'b1011: begin outSignal =7'b1100000;end
            4'b1100: begin outSignal =7'b0110001;end
            4'b1101: begin outSignal =7'b1000010;end
            4'b1110: begin outSignal =7'b0110000;end
            4'b1111: begin outSignal =7'b0111000;end
            default: begin outSignal =7'b0000000;end
        endcase
    end
endmodule

```

Top Module (Scramble Game)

// ECE6370

// Author: Sohail Shareef 5985

//Top level game module with authentication

module

Lab4_Sohail_M(button1,toggle1,rst,clk,ld1,ld2,switch_num2,green_led,red_led,sevens
eg_num2,sevens
eg_sum);

input[3:0] switch_num2;

input button1,ld1,ld2,rst,clk;

input [3:0] toggle1;

output[6:0] sevens
eg_num1, sevens
eg_num2, sevens
eg_sum;

output green_led, red_led;

wire[3:0] unscrambled_num, sum,Q_num1,Q_num2,Q_sum;

wire ld_1,ld_2,ld1_out,ld2_out,button_pulse;

wire [3:0] address,q;

wire [3:0] switch_num1;

button_shaper b1(button1, button_pulse, clk, rst);

//button_shaper ld1button(ld1,ld_1,clk, rst);

button_shaper ld2button(ld2,ld_2,clk, rst);

ROM_Top_Test rmt(address,clk, q);

access_control a1(button_pulse, toggle1,ld1, ld_2, red_led, green_led, ld1_out, ld2_out, clk,
rst,address,q);

unscramble unscramblenum2(switch_num2, unscrambled_num);

```

randomNumb(ld1_out,rst,clk,switch_num1);

load_register l1(switch_num1,Q_num1,ld1_out,clk,rst);
load_register l2(unscrambled_num,Q_num2,ld2_out,clk,rst);


adder addnums(Q_num1, Q_num2, sum);


seven_seg sevensegnum1(Q_num1, sevenseg_num1);
seven_seg sevensegnum2(Q_num2, sevenseg_num2);
seven_seg sevensegnum3(sum, sevenseg_sum);
endmodule

```

Counter

```

module counter(pulse,clk,rst,count);
    input clk,rst,pulse;
    output reg [3:0] count;
    //reg [3:0] count;

    always @(posedge clk)
        begin
            if(rst == 0)
                begin
                    count<=4'b0000;
                end
            else

```

```

        begin
            if(pulse==1) begin
                count <=count+4'b0001;
            end
        end

    end

end

endmodule

```

Button Inversion

```

// ECE6370
// Author: Sohail Shareef 5985
// This module is to create a button shapper ,which takes a low pulse
// to generate a single high pulse
module button_inv(button_push, button_pulse, clk, rst);
    //declaring inputs and outputs
    input button_push;
    output button_pulse;
    reg button_pulse;

    //clock and reset
    input clk,rst;

    //register to store state
    reg[2:0] state,state_next;
    parameter s_wait=0, state1=1;

```



```

always @ (posedge clk)
begin
    if(rst==0)
        button_pulse<=0;
    else
        if(button_push==0) begin
            button_pulse<=1;
        end
    else begin
        button_pulse<=0;
    end
end
endmodule

```

ROM Module:

```

`timescale 1 ps / 1 ps
// synopsys translate_on
module ROM_Top_Test (
    address,
    clock,
    q);

    input  [3:0] address;
    input  clock;
    output [3:0] q;
`ifndef ALTERA_RESERVED_QIS
// synopsys translate_off

```

```
`endif
```

```
    tri1    clock;
```

```
`ifndef ALTERA_RESERVED_QIS
```

```
// synopsys translate_on
```

```
`endif
```

```
    wire [3:0] sub_wire0;
```

```
    wire [3:0] q = sub_wire0[3:0];
```

```
    altsyncram    altsyncram_component (
```

```
        .address_a (address),
```

```
        .clock0 (clock),
```

```
        .q_a (sub_wire0),
```

```
        .aclr0 (1'b0),
```

```
        .aclr1 (1'b0),
```

```
        .address_b (1'b1),
```

```
        .addressstall_a (1'b0),
```

```
        .addressstall_b (1'b0),
```

```
        .byteena_a (1'b1),
```

```
        .byteena_b (1'b1),
```

```
        .clock1 (1'b1),
```

```
        .clocken0 (1'b1),
```

```
        .clocken1 (1'b1),
```

```
        .clocken2 (1'b1),
```

```
        .clocken3 (1'b1),
```

```
        .data_a ({4{1'b1}}),
```

```
        .data_b (1'b1),
```

```
        .eccstatus (),
```

```
        .q_b (),
```

```

        .rden_a (1'b1),
        .rden_b (1'b1),
        .wren_a (1'b0),
        .wren_b (1'b0));

defparam
    altsyncram_component.address_aclr_a = "NONE",
    altsyncram_component.clock_enable_input_a = "BYPASS",
    altsyncram_component.clock_enable_output_a = "BYPASS",
    altsyncram_component.init_file = "ROM_top.mif",
    altsyncram_component.intended_device_family = "Cyclone IV E",
    altsyncram_component.lpm_hint = "ENABLE_RUNTIME_MOD=NO",
    altsyncram_component.lpm_type = "altsyncram",
    altsyncram_component.numwords_a = 16,
    altsyncram_component.operation_mode = "ROM",
    altsyncram_component.outdata_aclr_a = "NONE",
    altsyncram_component.outdata_reg_a = "CLOCK0",
    altsyncram_component.widthad_a = 4,
    altsyncram_component.width_a = 4,
    altsyncram_component.width_byteena_a = 1;

endmodule

```

Access Module

```

// ECE6370
// Author: Sohail Shareef 5985
// This module is to create a access control to allow a validation of a 6 bit password
// by checking each bit and then produce a green light if all matches or red if

```

```

// any fail

module access_control(button_pulse, toggle_switch, ld1, ld2, red_led, green_led, ld1_out, ld2_out, clk,
rst,address,q);

input button_pulse,ld1, ld2;
input clk,rst;
input [3:0]toggle_switch,q;
output reg [3:0] address;
output reg ld1_out, ld2_out;
output reg red_led, green_led;

reg flag;
reg [2:0] state;
parameter s_wait=0,s1=1,s2=2,s3=3,s4=4,s5=5,s6=6,s7=7,s8=8;

always @ (posedge clk)
begin
if(rst==0) begin
state<=s_wait;
flag=1;
address <= 4'b0000;
end
else
begin
case(state)

s_wait:
begin

```

```
flag=1;
red_led<=0;
green_led<=0;
ld1_out<=1;
ld2_out<=0;
address <= 4'b0000;
if(button_pulse==1)
    state<=s1;
else
    state<=s_wait;
end
```

```
s1: begin
    red_led<=0;
    green_led<=0;

    if(button_pulse==1) begin
        address <= address+4'b0001;
        state<=s2;
    end
    else begin
        state<=s1;
    end
end
```

```
s2:
begin
    state<=s3;
end
```

s3:

begin

state<=s5;

end

s5:

begin

if(toggle_switch!=q) begin

flag=0;

end

if(address==4'b0100) begin

state<=s7;

end

else begin

state<=s1;

end

end

s7:

begin

if(flag==1)begin

red_led<=0;

green_led<=1;

if(ld1==1) begin

ld1_out<=1;

end

else begin

ld1_out=0;

end

```
        end
        else begin
            red_led<=1;
            green_led<=0;
        end
        if(ld2==1)
            ld2_out<=1;
        else ld2_out<=0;
        end
    default:
        state<=s_wait;
    endcase
end
end
endmodule
```

TEST BENCHES

Adder Test Bench

```
`timescale 1ns / 1ps
```

```
module Adder4bit_tb();
```

```
// Inputs
```

```
reg [3:0] A;
```

```
reg [3:0] B;
```

```
// Outputs
```

```
wire [3:0] Sum;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
initial begin
```

```
// Initialize Inputs
```

```
A  = 4'b0001;
```

```
B  = 4'b0110;
```

```
// Wait 100 ns for global reset to finish
```

```
#0.1;
```

```
// Add stimulus here
```

Scrambled Test Bench

```
`timescale 1ns / 1ps
```

```
module decoder_tb();
```



```
// Inputs
```

```
reg [3:0] A;
```

```
// Outputs
```

```
wire [6:0] Out7Signal;
```

```
decoder4to7 decodert (
```

```
    A,
```

```
    Out7Signal);
```

```
initial begin
```

```
// Initialize Inputs
```

```
A  = 4'b0001;#0.1;
```

```
A  = 4'b0110;#0.1;
```

```
A  = 4'b0111;#0.1;
```

```
A  = 4'b0100;#0.1;
```

```
A  = 4'b1010;#0.1;
```

```
A  = 4'b1011;#0.1;
```

```
A  = 4'b0010;#0.1;
```

```
A  = 4'b0101;#0.1;
```

```
A  = 4'b1110;
```

```
end  
endmodule
```

Decoder Test Bench

```
`timescale 1ns / 1ps
```

```
module decoder_tb();
```

```
// Inputs
```

```
reg [3:0] A;
```

```
// Outputs
```

```
wire [6:0] Out7Signal;
```

```
// Instantiate the Unit Under Test (UUT)
```

```
decoder4to7 decodert (
```

```
    A,
```

```
    Out7Signal);
```

```
initial begin
```

```
// Initialize Inputs
```

```
A  = 4'b0001;#0.1;

A  = 4'b0110;#0.1;
A  = 4'b0111;#0.1;
A  = 4'b0100;#0.1;
A  = 4'b1010;#0.1;
A  = 4'b1011;#0.1;
A  = 4'b0010;#0.1;
A  = 4'b0101;#0.1;
A  = 4'b1110;

//;

end
endmodule
```

Counter Test Bench :

```
// ECE6370
// Author: Sohail Shareef 5985
//testbench for counter
`timescale 1ns/100ps
module testb_counter();
    reg pulse, clk, rst;

    wire [3:0] count;
```

```
counter cntr(pulse,clk,rst,count);
```

```
always
```

```
begin
```

```
  clk <= 0;
```

```
  #10;
```

```
  clk <= 1;
```

```
  #10;
```

```
end // Note: Procedure repeats
```

```
// Vector Procedure
```

```
initial
```

```
begin
```

```
#3 rst=1;
```

```
#40 pulse =0;
```

```
#40 pulse =1;
```

```
#20 rst=0;
```

```
#40 pulse =0;
```

```
#40 pulse =1;
```

```
#40 rst =1;
```

```
#40 rst =0;
```

```
#70 rst=1;
```

```
end
```

```
endmodule
```

Button Inversion:

```
// ECE6370
```

```

// Author: Sohail SHareef 5985
//test bench for button_shaper
`timescale 1ns/100ps
module testbench_inversion ();
    reg button_push, clk, rst;
    wire button_pulse;

    button_inv tbtn(button_push, button_pulse, clk, rst);
    always
    begin
        clk <= 0;
        #10;
        clk <= 1;
        #10;
    end // Note: Procedure repeats
// Vector Procedure
initial
begin
    rst=1;
    button_push=1;
    @(posedge clk);
    @(posedge clk);
    button_push=0;
    @(posedge clk);
    @(posedge clk);
    button_push=1;
    @(posedge clk);
    @(posedge clk);
    @(posedge clk);

```

```

    @(posedge clk);
    @(posedge clk);
    rst=0;
    @(posedge clk);
    @(posedge clk);
    @(posedge clk);
    @(posedge clk);
    @(posedge clk);
    rst=1;
    button_push=0;
    @(posedge clk);
    button_push=1;
    @(posedge clk);
    @(posedge clk);
    button_push=0;
    end
endmodule

```

Top Module :

```

`timescale 10ns/100ps
module Test_overall();

    reg[3:0] switch_num2;
    reg button_pulse,ld1,ld2,rst,clk;
    reg [3:0] toggle_switch;
    wire[6:0] sevenseg_num1, sevenseg_num2, sevenseg_sum;
    wire green_led, red_led;
    // wire [3:0]address,q;

```

Lab4_Sohail_M

```
lab(button_pulse,toggle_switch,rst,clk,ld1,ld2,switch_num2,green_led,red_led,sevensseg_num1,sevensseg_num2,sevensseg_sum);
```

```
always begin
```

```
    #5 clk =0;
```

```
    #5 clk =1;
```

```
end
```

```
initial begin
```

```
    switch_num2 = 4'b1101;
```

```
    ld1=0;
```

```
    ld2=0;
```

```
    rst=0;
```

```
    ld1=0;
```

```
    ld2=0;
```

```
    rst=1;
```

```
    ld1=0;
```

```
    ld2=0;
```

```
    ld1=0;
```

```
    ld2=0;
```

```
    #15 button_pulse=0;
```

```
    #5 toggle_switch=4'b0001;
```

```
    #15 button_pulse=0;
```

```
#5 toggle_switch=4'b0010;
```

```
#15 button_pulse=0;
```

```
/*#5 toggle_switch=1;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
#5 button_pulse=0;
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
#5 toggle_switch=0;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
#5 button_pulse=0;
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
#5 toggle_switch=1;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```



```
#5 button_pulse=0;
```

```
#5 toggle_switch=0;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
#5 button_pulse=0;
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
#5 toggle_switch=1;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
#5 button_pulse=0;*/
```

```
#5 toggle_switch=4'b0011;
```

```
#15 button_pulse=1;
```

```
#5 toggle_switch=4'b0100;
```

```
#15 button_pulse=0;
```

```
end
```

```
endmodule
```

Random Number Test Bench :

```
// ECE6370
// Author: Sohail SHareef 5985
//test bench for button_shaper
`timescale 1ns/10ps
module testbench_randomNumber();
    reg pulse ;
    reg rst,clk;
    wire [3:0]count;

    randomNumb rnG(pulse,rst,clk,count);
    always
    begin
        clk <= 0;
        #10;
        clk <= 1;
        #10;
    end // Note: Procedure repeats
// Vector Procedure
    initial
    begin
        #3 rst=0;
```

```
#40 pulse =1;
#40 pulse =0;
#20 rst=1;
#40 pulse =1;
#40 pulse =0;
#40 rst =1;
#40 rst =1;
#70 rst=0;

end

endmodule
```

ROM MODULE TESTBENCH :

```
`timescale 10ns/100ps

module ROM_Testmodule();

reg    [3:0] address;
      reg    clk;
      wire   [3:0] q;

ROM_Top_Test rnd(
    address,
    clk,
    q);

always begin
    #5 clk =0;
    #5 clk =1;
```

```
end
```

```
initial begin
```

```
    address =4'b001;
```

```
#10 address =4'b010;
```

```
#10 address =4'b011;
```

```
#10 address =4'b101;
```

```
#10 address =4'b101;
```

```
#10 address =4'b111;
```

```
end
```

```
endmodule
```

Access Control Test Bench :

```
// ECE6370
```

```
// Author: Sohail Shareef 5985
```

```
//testbench for accesscontrol
```

```
`timescale 1ns/100ps
module testb_accesscontrol();
    reg button_pulse,ld1, ld2;
    reg clk,rst;
    reg [3:0]toggle_switch,q;
    wire [3:0] address;
    wire ld1_out, ld2_out;
    wire red_led, green_led;

    access_control acs(button_pulse, toggle_switch,ld1, ld2,
    red_led, green_led, ld1_out, ld2_out, clk, rst,address,q);
    always
    begin
        clk <= 0;
        #10;
        clk <= 1;
        #10;
    end // Note: Procedure repeats
// Vector Procedure
```

```
initial
begin
rst=0;
ld1=1;
ld2=1;
@(posedge clk);
rst=1;
@(posedge clk);
@(posedge clk);
@(posedge clk);
#15 button_pulse=1;
#5 toggle_switch=4'b1101;
q=4'b1101;
@(posedge clk);
#15 button_pulse=1;
@(posedge clk);
@(posedge clk);
@(posedge clk);
@(posedge clk);
@(posedge clk);
```

```
#5 toggle_switch=4'b1111;
```

```
q=4'b1111;
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
/*#5 toggle_switch=1;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
#5 button_pulse=0;
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
#5 toggle_switch=0;
```

```
@(posedge clk);
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
#5 button_pulse=0;
```

```
@(posedge clk);
```

```
@(posedge clk);  
@(posedge clk);  
@(posedge clk);  
@(posedge clk);  
#5 toggle_switch=1;  
@(posedge clk);  
#15 button_pulse=1;  
@(posedge clk);  
#5 button_pulse=0;  
@(posedge clk);  
@(posedge clk);  
@(posedge clk);  
@(posedge clk);  
@(posedge clk);  
#5 toggle_switch=0;  
@(posedge clk);  
#15 button_pulse=1;  
@(posedge clk);  
#5 button_pulse=0;  
@(posedge clk);
```



```
@(posedge clk);
@(posedge clk);
@(posedge clk);
#5 toggle_switch=1;
@(posedge clk);
#15 button_pulse=1;
@(posedge clk);
#5 button_pulse=0;*/
@(posedge clk);
@(posedge clk);
@(posedge clk);
@(posedge clk);
@(posedge clk);
@(posedge clk);
#5 toggle_switch=4'b1111;
q=4'b1111;
#15 button_pulse=1;
@(posedge clk);
@(posedge clk);
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
#5 toggle_switch=4'b1111;
```

```
q=4'b1111;
```

```
#15 button_pulse=1;
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
#5 ld1=1;
```

```
#5 ld2=1;
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
@(posedge clk);
```

```
end
```

```
endmodule
```